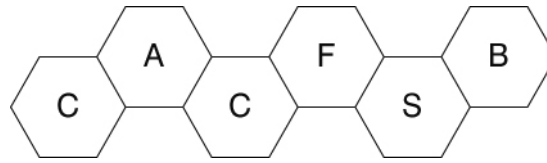


Name _____ Class _____ Date _____



- 1 a What C is the amount of electricity flowing around a circuit? _____
- b What A is the instrument that measures the amount of electricity? _____
- c What C makes electricity flow in a circuit? _____
- d What F is the part of a light bulb that glows? _____
- e What S is a component that can stop or start the current flowing? _____
- f What B is two or more cells used together? _____

2 Tick the boxes to show if each statement is true or false.

	True	False
a If one bulb breaks in a simple circuit, the other bulbs will go off.	<input type="checkbox"/>	<input type="checkbox"/>
b Current gets used up as it goes around a circuit.	<input type="checkbox"/>	<input type="checkbox"/>
c If you put more bulbs into a circuit they will get brighter.	<input type="checkbox"/>	<input type="checkbox"/>
d A cell is the same thing as a battery.	<input type="checkbox"/>	<input type="checkbox"/>

3 Draw the correct circuit symbols in the boxes.

cell	ammeter	bulb	switch

I can...

- draw the symbols for some circuit components
- describe what happens when more bulbs are added to a circuit
- describe what a current is and how it is measured.